

Nama :

DPP B2(c)

Kelas :

LABORATORY REPORT



MARA JAPAN INDUSTRIAL INSTITUTE
BERANANG
LOT 2333, JALAN KAJANG-SEREMBAN
43700 BERANANG
SELANGOR DARUL EHSAN


JS02

COURSE/CLASS :	DIPLOMA IN ELECTRONICS ENGINEERING		
SESSION :		SEMESTER :	3
CODE/SUBJECT :	DFV31153 / ANALOGUE ELECTRONIC 2	SHEET NO :	JS 02
NO OF STUDENTS :		WEEK :	
DURATION :	3 hour	VENUE :	Electronic Devices Lab
LECTURER :			

TOPIC :	POWER SUPPLY (VOLTAGE REGULATOR)
SUB-TOPIC :	VOLTAGE REGULATOR CIRCUIT
LEARNING OUTCOME :	At the end of the lesson, students should be able to : 1. Measure the dc output voltages of resistor load. 2. Study the performance of simple series regulator, shunt voltage regulator and IC regulator.

TOOLS / EQUIPMENTS / MATERIALS :	INSTRUMENTS : 1. Digital Multimeter 2. Edibon Development Module (M15) 3. Edibon Power Supply Module (M5) COMPONENTS : 1. 2N3904 - 2 2. 1N5327 8.2 V – Zener diode - 2 3. Resistor 1kΩ - 2 4. Resistor 3.3kΩ - 2
---	--


PROCEDURE

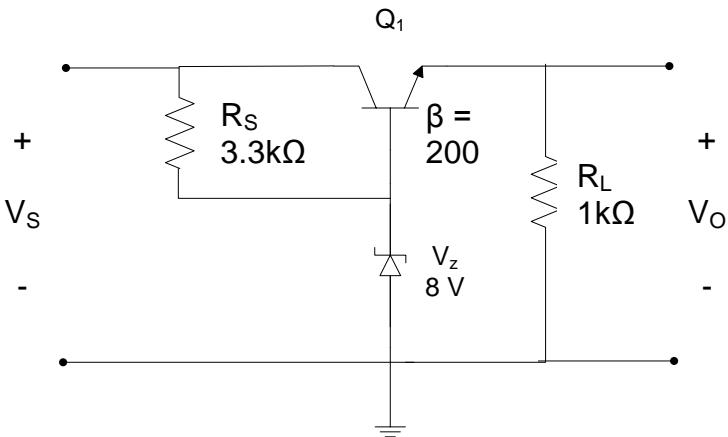STEP	KEY POINT
PART 1: Series Voltage regulator.	<ol style="list-style-type: none"> 1. Calculate the output voltage and zener current in Figure 1 for input voltage, $V_S = 4V, 6V, 8V, 10V$ and $12V$ 2. Simulate circuit in Figure 1 using MULTISIM software. 3. Assemble circuit as Figure 1. 4. Vary V_S, measure and record the output voltage V_O in table 1.  <p style="text-align: center;">Figure 1.1</p>

RESULT (PART 1)

V_{in}	4V	6V	8V	10V	12V
V_O Calculated					
I_z Calculated					
V_O Simulated					
I_z Simulated					
V_O Measured					
I_z Measured					

TABLE 1

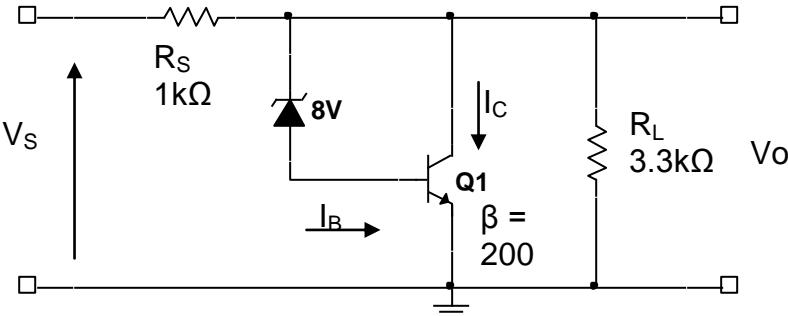STEP	KEY POINT
PART 2: Shunt voltage regulator circuit.	<ol style="list-style-type: none"> Calculate the output voltage and transistor current in Figure 2 for input voltage, $V_S = 4V, 6V, 8V, 10V$ and $12V$ Simulate circuit in Figure 2 using MULTISIM software. Assemble circuit as Figure 2. Vary V_S, measure and record the output voltage V_O in table 2.  <p>Figure 2</p>

RESULT (PART 2)

V_{in}	4V	6V	8V	10V	12V
V_O Calculated					
I_C calculated					
V_O Simulated					
I_C Simulated					
V_O Measured					
I_C Measured					

Table 2

DISCUSSION

1. Sketch output voltage, V_O against input voltage, V_S for part 1 and part 2
2. Discuss your finding in Part 1 and Part 2
3. Compare the data using the values obtain in Part 1 and Part 2. Comment the regulation behavior for each circuit.

CONCLUSION

PROGRAMME :	DIPLOMA IN ELECTRONIC ENGINEERING (DKC,DKE,DKM,DKR,DKS)						DURATION:
TOPIC:	JOBSHEET 1/2/3/4/5/6						2 HOURS
COURSE:	DFV31153 ANALOGUE ELECTRONICS 2						WEIGHTAGE:
RELATED CLO:	Display the skill to conduct experiments on electronic devices circuit. (PLO4, P4)						20%
STUDENT NAME :							
SEM / SESSION :							

SECTION A: CRITICAL ASSESSMENT

No.	Mark ✓ for type of critical item to be assessed.						Mark ✓ = YES if follow the criteria	
	1. Functional	2. Accuracy	3. Finishing	4. Agility	5. Endurance	6. Safety	Mark X = NO if not follow the criteria	
							YES	NO
1	No critical items						✓	

SECTION B: WORKING PROCESS ASSESSMENT [100%]

No.	Criteria			Basic Mark	Factor / FP	Obtain Basic Mark	Obtain Mark			
WORK PROCESS										
PLANNING (DP1- DK6 : PRACTICAL ENGINEERING KNOWLEDGE)										
1	CLO2: P4	1.1	Able to translate & interpret facts in the experimental context.							
			i) Not able to read or interpret the procedure	0	0.67					
			ii) Poor to read or interpret the procedure but with guidance	1						
			iii) Able to read or interpret the procedure but with guidance	2						
			iv) Able to read or interpret the procedure which occupy to specification without guidance.	3						
Calculate parameter value (DP2 : RANGE OF CONFLICTING)										
2	CLO2: P4	2.1	i) Not able to do the task	0	1.33					
			ii) Able to calculate and applying formulae / theorem but not complete	1						
			iii) Able to calculate and applying formulae/ theorem to proof theoretical expected value but not correctly	2						
			iv) Able to calculate and applying formulae/ theorem to proof theoretical expected value correctly and precisely	3						
Skills of Handling Instrument/ Tools (DP2 : RANGE OF CONFLICTING)										
2	CLO2: P4	2.2	i) Poor to handle tools/ equipment	1	1.33					
			iii) Able to handle tools /equipment correctly with guidance	2						
			iii) Able to use tools/ equipment and equipment correctly without guidance	3						
Measurement Method (DP2 : RANGE OF CONFLICTING)										
2	CLO2: P4	2.3	i) Poor to apply measurement method	1	1.33					
			iii) Able to apply measurement method correctly with guidance (eg: voltage-in parallel; current- in series)	2						
			iii) Able to apply measurement method correctly without guidance	3						

RESULT / OUTCOME / SKILLS

DOMAIN	DATA RECORDING/ RESULT (DP3- DEPTH OF ANALYSIS)					
Data Recording						
3	CLO2: P4	3.1	i) Not able to do the task	0	0.67	
			iii) Able to record PART of data and observation in logbook / prepare lab sheet	1		
			iii) Able to record ALL data and observation in logbook / prepare lab sheet	2		
			iii) Able to record ALL the relevant and vital data and observation in logbook / prepare lab sheet completely according to spesifications (complete unit) and neatness	3		
Component / Electrical parameter measurement						
3	CLO2: P4	3.2	i) More / Less ± 50% from exact value (out of range)	0	1.00	
			ii) Almost accurate (within acceptable range)	1		
			iii) Accurate	2		
Complying the tasks / questions given or produce graph						
3	CLO2: P4	3.3	i) Not able to do the task	0	0.67	
			ii) Able to comply the tasks / questions given but not completely	1		
			iii) Able to comply the tasks / questions given completely	2		
			iv) Able to comply the tasks / questions given completely according to spesifications	3		

Obtain Marks

Total Marks

100.0

Total Marks 20%

VERIFICATION

SIGNATURE & OFFICIAL STAMP:

DATE:

Edition 3.0 / 2021